

HW 11

29-31 Coil $N = 350$

$d = 10.0 \text{ cm}$

$f = 60 \text{ rev/s}$

$B = 0.45 \text{ T}$

29-37

transformer

$V_p = 120 \text{ V}$, $N_p = 500$

$V_s = 8500 \text{ V}$

from 29-5

$$V_{\text{rms}} = \frac{\mathcal{E}_0}{\sqrt{2}}$$

$$= \frac{NBA\omega}{\sqrt{2}}$$

$$\text{where } A = \pi d^2 = \pi (0.50 \times 10^{-1} \text{ m})^2$$

$$\omega = 2\pi f$$

so

$$V_{\text{rms}} = \frac{(350)(0.45 \text{ T})(0.50 \times 10^{-1} \text{ m})^2 \times (2\pi)^2}{\sqrt{2}}$$

$$= 3.30 \times 10^2 \text{ V}$$

V_{rms} is proportional to ω , so to double V_{rms} , we should double ω , or equivalently f

$60 \text{ rev/s} \rightarrow 120 \text{ rev/s}$

$$\frac{V_s}{V_p} = \frac{N_s}{N_p} \Rightarrow N_s = N_p \frac{V_s}{V_p} = 500 \frac{8500}{120} = 3.54 \times 10^4$$

30-16

29-39 Step-up transformer

$$V_p = 22 \text{ V}$$

$$V_s = 120 \text{ V}$$

use (29-5)

$$\frac{V_s}{V_p} = \frac{N_s}{N_p} = \frac{120}{22}$$

and (29-6)

$$\frac{N_p}{N_s} = \frac{I_s}{I_p}$$

to get

$$\frac{V_s}{V_p} = \frac{I_p}{I_s} = \frac{120}{22}$$


$$\text{or } \frac{I_s}{I_p} = \frac{22}{120} = 0.18$$

we could also use that power on both sides is same.

$$I_s V_s = I_p V_p$$

to get directly

$$\frac{I_s}{I_p} = \frac{V_p}{V_s}$$

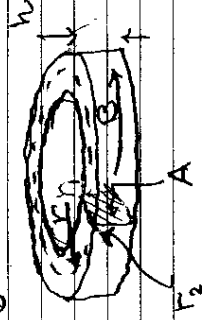

$\vec{B}$ is $\perp$ to A , $\downarrow$ flux

Need to know Φ_B through surface A

$\vec{B}$ is $\perp$ to A ,

$$\Phi_B = \int \vec{B} \cdot d\vec{A} = B \times \int_{r_2}^{r_1} B \omega dr$$

To get B use Ampere's law to circular path of radius r

$$\int \vec{B} \cdot d\vec{l} = \frac{I_{\text{enc}}}{\mu_0}$$

$$B(2\pi r) = \mu_0 NI$$


$$B = \frac{\mu_0 NI}{2\pi r}$$

Then

$$\Phi_B = \frac{\mu_0 NI}{2\pi} h \int_{r_1}^{r_2} \frac{1}{r} dr$$

$$= \frac{\mu_0 NI h \ln \frac{r_2}{r_1}}{2\pi}$$
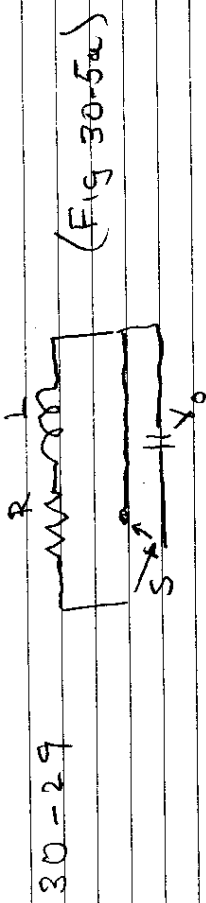
$$\text{Self Inductance: } L = \frac{N \Phi}{I} = \frac{\mu_0 N^2 h \ln \frac{r_2}{r_1}}{2\pi}$$



a) Energy stored in L as a function of time.

Current in circuit (after S connects V_0)

$$(Eq (30-9)) \quad I = \frac{V_0}{R} (1 - e^{-t/\tau})$$

where $\tau = \frac{L}{R}$ is the time constant

$$U_L = \frac{1}{2} L I^2 \quad (Eq 30-6)$$

$$= \frac{1}{2} \frac{L V_0^2}{R^2} (1 - e^{-t/\tau})^2$$

b) when is $U_L = 0.99 U_{max}$?

$$0.99 U_{max} = \left(\frac{L V_0^2}{2 R^2} \right) (1 - e^{-t/\tau})^2$$

$$0.99 = (1 - e^{-t/\tau})^2$$

$$1 - e^{-t/\tau} = \sqrt{0.99}$$

$$e^{-t/\tau} = 1 - \sqrt{0.99} = 5.01 \times 10^{-3}$$

$$t = -\tau \ln(5.01 \times 10^{-3}) = 5.3 \tau$$

30-35 LC circuit

$$Q = Q_0 \text{ at } t=0$$

At first time when

$$U_E = U_B$$

τ E in capacitor, τ E in inductor
Call this t_0

$$a) \quad Q(t) = Q_0$$

$$Q(t) = Q_0 \cos(\omega t + \phi)$$

$$\text{so } \phi = 0$$

then from page 764

$$U_E = U_B \text{ says}$$

$$\frac{Q^2}{2C} \cos^2 \omega t = \frac{Q_0^2}{2C} \sin^2 \omega t$$

need first t_0 for which

$$\cos^2 \omega t_0 = \sin^2 \omega t_0$$

which is $\omega t_0 = \pi/4 \rightarrow t_0 = \frac{\pi}{4\omega}$

$$\text{then } Q(t_0) = Q_0 \cos \frac{\pi}{4} = \frac{Q_0}{\sqrt{2}}$$

$$b) \quad t_0 = \frac{\pi}{4\omega} = \left(\frac{2\pi}{\omega} \right) \frac{1}{4} = \left(\frac{T}{2} \right) \frac{1}{4} = \frac{T}{8}$$

with T the period