

HW 12

31-2 $L = 22.0 \text{ mH} = 2.2 \times 10^{-2} \text{ H}$


$X_L = \omega L = 6.60 \times 10^2 \Omega$

$\omega = \frac{X_L}{L}$

$f = \frac{\omega}{2\pi} = \frac{X_L}{2\pi L} = \frac{6.60 \times 10^2 \Omega}{(6.28)(2.2 \times 10^{-2} \text{ H})}$

$= (0.478) \times 10^4 \text{ Hz}$

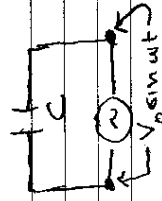$= 4.78 \times 10^3 \text{ Hz} = 4.78 \text{ kHz}$



31-9(a) $V = V_0 \sin \omega t$

$V(t) = \frac{Q(t)}{C}$

$Q(t) = C V(t) = C V_0 \sin \omega t$

$I(t) = \frac{dQ(t)}{dt} = \omega C V_0 \cos \omega t$

$\frac{d}{dt} \sin \omega t = \cos \omega t$

because: $\sin(\omega t + 90^\circ) = \sin \omega t \cos \frac{\pi}{2}$

also have: $\cos \omega t = \sin(\omega t + 90^\circ)$

$I(t) = \omega C V_0 \sin(\omega t + 90^\circ)$

31-19 For coil $Z = 335 \Omega$

$X_L = 45.5 \Omega$

Now treat the coil as part of an LRC circuit with $X_C = 0$. In general

$Z = \sqrt{R^2 + (X_L - X_C)^2}$

So now

$Z = \sqrt{R^2 + X_L^2}$

$R = \sqrt{Z^2 - X_L^2}$

$= \sqrt{(335 \times 10^2)^2 - (45.5 \times 10^2)^2} \Omega$

$= 332 \Omega$

31-23 LRC circuit

$$L = 32.0 \text{ mH}$$

$$R = 8.70 \text{ k}\Omega$$

$$C = 5000 \text{ pF}$$

$$V_{\text{rms}} = 800 \text{ V}$$

$$f = 10.0 \text{ kHz}$$

31-25 LRC circuit of Example 31-3

$$L = 30.0 \text{ mH}$$

$$C = 12.0 \text{ }\mu\text{F}$$

resonant frequency

$$f_0 = \frac{\omega}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{(6.28)(30.0 \times 10^{-3} \text{ H} \times 12.0 \times 10^{-6} \text{ F})^{1/2}}$$

$$= (2.65 \times 10^{-2}) \times 10^4 \text{ Hz}$$

$$= 2.65 \times 10^2 \text{ Hz}$$

$$= 265 \text{ Hz}$$

$$\omega = 2\pi f = 62.8 \text{ kHz}$$

$$X_L = \omega L = (62.8 \times 10^3)(32.0 \times 10^{-3}) \Omega$$

$$= 2.01 \times 10^3 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(62.8 \times 10^3)(5.00 \times 10^{-9} \times 10^{-12}) \Omega}$$

$$= 3.18 \times 10^{-3} \times 10^6 \Omega$$

$$E_9(31-9a) = 3.18 \times 10^3 \Omega$$

Impedance

$$Z = \sqrt{(8.70 \times 10^3)^2 + (2.01 \times 10^3 - 3.18 \times 10^3)^2} \Omega$$

$$E_9(31-10a) = 8.78 \times 10^3 \Omega = 8.78 \text{ k}\Omega$$

Phase angle

$$\tan \phi = \frac{X_L - X_C}{R} = \frac{1.17 \text{ k}\Omega}{8.78 \text{ k}\Omega} = -0.134$$

$$(p. 779) \rightarrow \phi = -7.63^\circ$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{8 \times 10^2 \text{ V}}{8.78 \times 10^3 \Omega} = 9.11 \times 10^{-2} \text{ A}$$

32-9 $E_0 = 0.43 \times 10^{-4} \frac{V}{m}$
for wave

$$B_0 = \frac{E_0}{c}$$

$$= \frac{0.43 \times 10^{-4} \frac{V}{m}}{3.0 \times 10^8 \frac{m}{s}}$$

$$= 0.14 \times 10^{-12} T$$

32-11 $E_x = E_0 \cos(kz + \omega t)$

$$E_y = E_z = 0$$

$B_0 = \frac{E_0}{c}$ (see Ex 32-3) b) $\cos(kz + \omega t)$

↑ wave is moving in $-\hat{z}$ -direction

a) B must be perp. to $\vec{E}$ and direction of motion

B_y is only non-zero component

$$\Rightarrow B_y^{\max} = B_0 = \frac{E}{c}$$

$$B_x = B_z = 0$$

direction of propagation is given by $\vec{E} \times \vec{B}$

direction of wave is $-\hat{k}$

then we have $\vec{E} = \hat{i} E_0 \cos(kz + \omega t)$

$$\vec{B} = -\hat{y} B_0 \cos(kz + \omega t)$$

because $\hat{i} \times (-\hat{y}) = -\hat{k}$