

HW 6

25-47 $\overline{P} = 1800 \text{ W}$




26-11

$V_{\text{rms}} = 450 \text{ V}$

$I_{\text{rms}} = \frac{P}{V_{\text{rms}}} = 4 \text{ A}$

$I_{\text{peak}} = I_0 = \sqrt{2} I_{\text{rms}} = 5.66 \text{ A}$

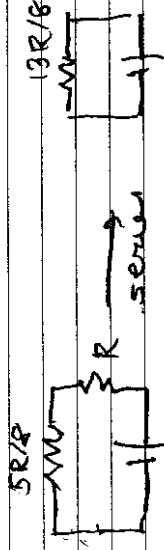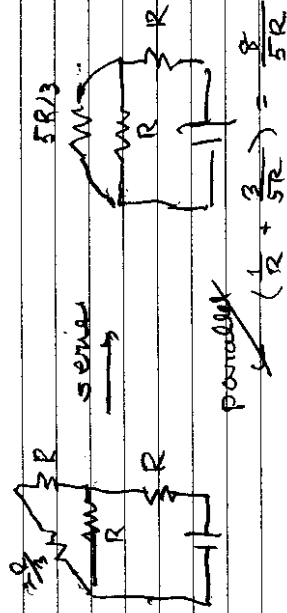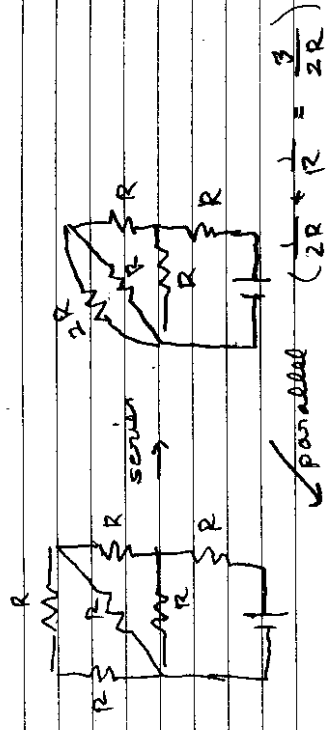$V_{\text{peak}} = V_0 = \sqrt{2} V_{\text{rms}} = 636 \text{ V}$




$R_{\text{eq}} = \frac{12}{8} R = \frac{13}{8} (2.8 \text{ k}\Omega) = 4.6 \text{ k}\Omega$

26-26

2 in 3 →

$$V_1 = 9V, R_1 = 22\Omega$$

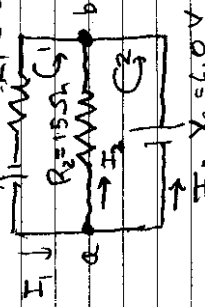

Kirchoff:

$$I_1 = I_2 + I_3 \quad \text{at both junctions}$$

For the two loops shown
add in voltage drop for
internal resistance, $r = r_3 = 1.2\Omega$

Get:

$$V_1 - I_1 r_1 - I_2 R_2 - I_1 R_1 = 0$$

$$9.0V - I_2(15\Omega) - I_1(23.2\Omega) = 0$$

$$\text{notice } \rightarrow V_3 - I_3 r_3 + I_2 R_2 = 0$$

$$+ I_2 R_2 \text{ opposite} \rightarrow 6.0V - I_3(1.2\Omega) + I_2(15\Omega) = 0$$

(in drop direction)

Have to solve the three equations marked by "✓"

Have

$$I_2 = -0.33A \text{ etc.}$$

$$\text{Then } I_3 = I_1 - I_2 = 0.93A$$

$$6.0 - (I_1 - I_2)(1.2) + I_2(15) = 0$$

$$-I_1(1.2) = -6.0 - I_2(16.2)$$

$$I_1 = \frac{6.0}{1.2} + I_2 \left(\frac{16.2}{1.2} \right)$$

$$I_1 = 5.0 + I_2(13.5)$$

put in 6/

$$9.0 - I_2(15) - (5.0 + I_2(13.5))(23.2) = 0$$

$$I_2(-13.5 \times 23.2 - 15) + (9.0 - 5 \times 23.2) = 0$$

$$I_2(-328.2) - 107 = 0$$


$$I_2 = -0.33A$$

Then can get I_1 from 6/

$$9.0V - (-0.33)(15)V - I_1(23.2\Omega) = 0$$

$$I_1 = 0.60A$$

$$R = 15 \text{ k}\Omega$$

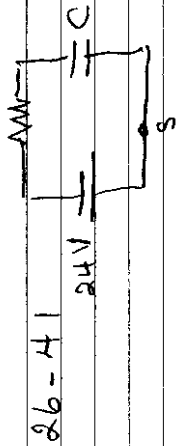

$$a) \tau = RC = 55 \mu\text{s}$$

$$= 5.5 \times 10^{-5} \text{ s}$$

$$C = \frac{5.5 \times 10^{-5} \text{ s}}{1.5 \times 10^4 \Omega}$$

$$= 3.67 \times 10^{-9} \text{ F}$$

$$= 3.67 \text{ nF}$$

b) Time for voltage across R to reach 16V

Use

$$16.0 \text{ V} = V = \frac{E}{R} e^{-t/RC}$$

$$= \frac{E}{R} e^{-t/RC}$$

$$-t/RC$$

$$16.0 \text{ V} = 24 \text{ V} e^{-t/RC}$$

$$\frac{2}{3} = e^{-t/RC}$$

$$\ln \frac{2}{3} = -t/RC \rightarrow t = 5.5 \times 10^{-5} \text{ s} \cdot \ln \frac{3}{2}$$

$$-\ln \frac{2}{3} \quad 5.5 \times 10^{-5} \text{ s} \quad t = 2.2 \times 10^{-5} \text{ s}$$